

3.

$$a) C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12})(.082^2 \pi)}{.0013}$$

$$C = 144 \times 10^{-12} \text{ F} = 144 \text{ pF}$$

$$b) Q = CV = (144 \text{ pF})(120 \text{ V}) = 17.3 \times 10^{-9} \text{ coulombs}$$

$$\text{or } Q = 17.3 \text{ nC}$$

6.

$$a) C = \frac{\epsilon_0 A}{d}$$

$$1 \text{ F} = \frac{(8.85 \times 10^{-12})(1 \text{ m}^2)}{d}$$

$$d = 8.85 \times 10^{-12} \text{ m}$$

b) This is not possible. The plates would not stay separated.

10.

$$\frac{1}{C_{\text{eq}}} = \frac{1}{10 + 5} + \frac{1}{4} = \frac{4}{60} + \frac{15}{60}$$

$$C_{\text{eq}} = \frac{60}{19} = 3.2 \mu \text{ F}$$

11.

$$C = \frac{Q}{V} = \frac{1.0 \text{ C}}{110 \text{ V}} = .0091 \text{ F}$$

$$n(1 \times 10^{-6} \text{ F}) = .0091 \text{ F}$$

$$n = 9100$$

13.

$$100 \times 10^{-12} \text{ F} = \frac{Q}{50 \text{ V}}$$

$$Q = 5000 \times 10^{-12} \text{ coulombs}$$

Charge must be conserved.

$$Q_0 = Q_1 + Q_2$$

$$C_1 V_0 = C_1 V + C_2 V$$

$$V = \frac{C_1 V_0}{C_1 + C_2} = 50 \left(\frac{C_1}{C_1 + C_2} \right)$$

$$V = 35 = 50 \left(\frac{100 \times 10^{-12}}{100 \times 10^{-12} + C_2} \right)$$

$$100 \times 10^{-12} + C_2 = \left(\frac{50}{35} \right) (100 \times 10^{-12})$$

$$C_2 = 42 \times 10^{-12} = 42 \text{ pF}$$

17. Refer back to problem #16. The subscripts match the capacitor's number.

$$V_3 = \frac{320 \mu\text{C}}{4 \mu\text{F}} = 80 \text{ volts}$$

$$\therefore V_1 = V_2 = 20 \text{ volts}$$

Change in C_1 :

$$\Delta V_1 = 100 - 20 = 80 \text{ volts}$$

$$Q = CV$$

$$\text{final: } Q = (100 \text{ V})(10 \mu\text{F}) = 1000 \mu\text{C}$$

$$\text{initial: } Q = (20 \text{ V})(10 \mu\text{F}) = 200 \mu\text{C}$$

$$\Delta Q = 1000 - 200 = 800 \mu\text{C}$$

27.

a) S_1 closed. C_1 and C_3 are in series.

$$\frac{1}{C_{\text{Top}}} = \frac{1}{C_1} + \frac{1}{C_3} = \frac{1}{1} + \frac{1}{3} = \frac{4}{3}$$

$$C_{\text{Top}} = \frac{3}{4} \mu\text{F}$$

C_2 and C_4 are in series.

$$\frac{1}{C_{\text{Bottom}}} = \frac{1}{C_2} + \frac{1}{C_4} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4}$$

$$C_{\text{Bottom}} = \frac{4}{3} \mu\text{F}$$

C_{Top} and C_{Bottom} are in parallel.

$$C_{\text{Eq}} = \frac{3}{4} + \frac{4}{3} = 2.1 \mu\text{F}$$

$$Q = CV = 2.1(12\text{V}) = 25 \mu\text{C}$$

$$Q = C_{\text{Top}} V = .75(12) = 9 \mu\text{C}$$

$$Q = C_{\text{Bottom}} V = 1.33(12) = 16 \mu\text{C}$$

C_1 and C_3 have $9 \mu\text{C}$ charge each.

C_2 and C_4 have $16 \mu\text{C}$ charge each.

b) S_2 closed, potentials now equal.

C_1 and C_2 are in parallel.

$$C_{1-2} = C_1 + C_2 = 3 \mu\text{F}$$

C_3 and C_4 are in parallel.

$$C_{3-4} = C_3 + C_4 = 7 \mu\text{F}$$

C_{1-2} and C_{3-4} are in series.

$$\frac{1}{C_{\text{Eq}}} = \frac{1}{C_{1-2}} + \frac{1}{C_{3-4}} = \frac{1}{3} + \frac{1}{7}$$

$$C_{\text{Eq}} = 2.1 \mu\text{F}$$

$$Q = CV = 2.1(12) = 25 \mu\text{C}$$

$$V_{1-2} = \frac{25}{3} = 8.3 \text{ and } V_{3-4} = \frac{25}{7} = 3.6$$

$$Q_1 = (1 \mu\text{F})(8.3\text{V}) = 8.3 \mu\text{C}$$

$$Q_2 = (2 \mu\text{F})(8.3\text{V}) = 16.6 \mu\text{C}$$

$$Q_3 = (3 \mu\text{F})(3.6\text{V}) = 10.8 \mu\text{C}$$

$$Q_4 = (4 \mu\text{F})(3.6\text{V}) = 14.4 \mu\text{C}$$

31.

$$U = \frac{1}{2}CV^2$$

$$C = C_1 + C_2 = 2 + 4 = 6\mu\text{F}$$

$$U = \frac{1}{2}(6\mu\text{F})(300\text{V})^2$$

$$U = .27\text{joules}$$

33.

$$V = \frac{kq}{r}$$

$$8000 = \frac{kq}{.05\text{m}}$$

$$\therefore q = \frac{400}{k}$$

$$E = \frac{kq}{r^2} = \frac{k\left(\frac{400}{k}\right)}{(.05)^2}$$

$$E = 1.6 \times 10^5$$

$$U = \frac{1}{2}\epsilon_0 E^2 = \frac{1}{2}(8.85 \times 10^{-12})(1.6 \times 10^5)^2$$

$$U = .1133 \frac{\text{joules}}{\text{meters}^3}$$

42.

$$\text{a) } C = \frac{\epsilon_0 A}{d}$$

$$50 \times 10^{-12} = \frac{(8.85 \times 10^{-12})(.35)}{d}$$

$$d = 6.2\text{cm}$$

$$\text{b) } C = kC_0 = 5.6(50 \times 10^{-12})$$

$$C = 280 \times 10^{-12} = 280\text{pF}$$

43.

Got 7.4pF, want 7.4μJ.

$$U = \frac{1}{2} CV^2 = 7.4\mu\text{J}$$

$$\frac{1}{2} C(652)^2 = 7.4$$

$$C = 35\text{pF}$$

$$\frac{35\text{pF}}{7.4\text{pF}} = 4.7$$

Pyrex is a good choice.

51.

$$\text{a) } E = \frac{E_0}{k} = \frac{Q}{k\epsilon_0 A}$$

$$Q = CV$$

$$E = \frac{CV}{k\epsilon_0 A} = \frac{(100 \times 10^{-12})(50)}{5.4(8.85 \times 10^{-12})(.01\text{m}^2)}$$

$$E = \frac{5000 \times 10^{-12}}{.48 \times 10^{-12}} = 10,000 \frac{\text{volts}}{\text{meter}}$$

b) Free charge:

$$q = C_0 V_0 = (100 \times 10^{-12})(50)$$

$$q = 5 \times 10^{-9} \text{ C}$$

c) Induced charge:

$$q' = q \left(1 - \frac{1}{k}\right) = (5 \times 10^{-9}) \left(1 - \frac{1}{5.4}\right)$$

$$q' = 4.7 \times 10^{-9} \text{ C}$$

53.

$$a) C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12})(.12m^2)}{.012m} = 89pF$$

b) Dielectric fills $\frac{1}{3}$ the space. $V = Ed$

$$V = E_0 \left(\frac{2}{3}d \right) + \frac{E_0}{k} \left(\frac{1}{3}d \right) = E_0 d \left(\frac{2}{3} + \frac{1}{3k} \right) = V_0 \left(\frac{2k+1}{3k} \right)$$

$$V = 120 \left(\frac{10.6}{14.4} \right) = 88.3 \text{volts}$$

$$\text{need } Q = C_0 V_0 = (89pF)(120V) = 10.7nC$$

$$C = \frac{10.7nC}{88.3V} = 120pF$$

$$c) Q = C_0 V_0 = (89pF)(120V) = 10.7nC$$

$$d) E_0 = \frac{Q}{\epsilon_0 A} = \frac{10.7 \times 10^{-9}}{(8.85 \times 10^{-12})(.12)} = 10 \frac{\text{kilovolts}}{\text{meter}}$$

$$e) E = \frac{Q}{k\epsilon_0 A} = \frac{10.7 \times 10^{-9}}{(4.8)(8.85 \times 10^{-12})(.12)} = 2083 \frac{\text{volts}}{\text{meter}}$$

f) From above $V = 88.3 \text{volts}$, or $V = \frac{Q}{C}$ where $C = 120pF$.

$$g) U_0 = \frac{1}{2} C_0 V_0^2 = \frac{1}{2} (89)(120)^2 = .641 \mu j$$

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (120)(88.3)^2 = .468 \mu j$$

$$W = .641 - .468 = .173 \mu j$$

67. a) The charge must be the same for each capacitor.

$$\frac{1}{C} = \frac{1}{6} + \frac{1}{4} = \frac{2+3}{12} = \frac{5}{12}$$

$$C = 2.4 \mu F$$


$$C = \frac{Q}{V} \Rightarrow Q = CV$$

$$Q = 2.4(200) = 480 \mu C$$

$$V_1 = \frac{Q}{C_1} = \frac{480 \mu C}{6 \mu F} = 80 \text{volts}$$

$$V_2 = \frac{Q}{C_2} = \frac{480 \mu C}{4 \mu F} = 120 \text{volts}$$
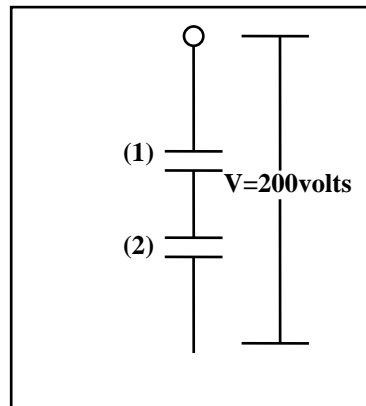
$$\text{Check: } 120 + 80 = 200 \text{volts}$$



68. The potential across each is 200 volts.

$$C = 6 + 4 = 10\mu\text{F}$$

$$Q_1 = C_1 V_1 = 6(200) = 12 \times 10^{-4} \text{ C}$$

$$Q_2 = C_2 V_2 = 4(200) = 8 \times 10^{-4} \text{ C}$$

70.

$$C = \frac{\epsilon_0 A}{d}, \text{ if capacitor is empty.}$$

d is now reduced by **b**, the thickness of the metal.

$$\text{a) } C = \frac{\epsilon_0 A}{d - b}$$

$$\text{b) } W(\text{empty}) = \frac{1}{2} C_E V^2 = \frac{1}{2} \frac{Q^2}{C_E}$$

$$W(\text{full}) = \frac{1}{2} C_F V^2 = \frac{1}{2} \frac{Q^2}{C_F}$$

$$\frac{W(\text{empty})}{W(\text{full})} = \frac{C_F}{C_E} = \frac{\left(\frac{\epsilon_0 A}{d - b}\right)}{\left(\frac{\epsilon_0 A}{d}\right)} = \frac{d}{d - b}$$

c) Must be the difference $W(\text{full}) - W(\text{empty})$.

$$\frac{1}{2} \frac{Q^2}{\left(\frac{\epsilon_0 A}{d}\right)} - \frac{1}{2} \frac{Q^2}{\left(\frac{\epsilon_0 A}{d - b}\right)} = \frac{1}{2} \frac{Q^2 d}{\epsilon_0 A} - \frac{1}{2} \frac{Q^2 (d - b)}{\epsilon_0 A}$$

$$= \frac{1}{2} \frac{Q^2}{\epsilon_0 A} (d - (d - b)) = \frac{1}{2} \frac{Q^2 b}{\epsilon_0 A}$$

The slab is sucked in.

72.

$$\text{a) } \frac{1}{C} = \frac{1}{2} + \frac{1}{8} = \frac{4+1}{8}$$

$$C_{\text{eq}} = 1.6\mu\text{F}$$

$$Q = CV = (1.6\mu\text{F})(300\text{V}) = 480\mu\text{C}$$

b) Now there is $2(480) = 960\mu\text{C}$ to divide up.

$$\left(\frac{2}{10}\right)(960) = 192\mu\text{C}$$

$$\left(\frac{8}{10}\right)(960) = 770\mu\text{C}$$

$$\text{Voltages? } V = \frac{Q}{C}$$

$$V_2 = \frac{192\mu\text{C}}{2\mu\text{F}} = 96\text{volts}$$

$$V_8 = \frac{770\mu\text{C}}{8\mu\text{F}} = 96\text{volts}$$

c) Now the charges cancel each other out.

$$Q = V = 0$$