

1.

- a) Current flows from B to A.
- b) The 12 volt battery is doing positive work.
- c) B is at a higher potential.

2.

Need I first.

$$I = \frac{\sum \mathcal{E}}{\sum R} = \frac{100}{5} = 20 \text{ amps}$$

$$V_Q + 150 - 20(2\Omega) = V_P = 100$$

$$V_Q = -10 \text{ volts}$$

5.

$$5 \text{ amps} = 5 \frac{\text{coul}}{\text{sec}}$$

$$6 \text{ volts} = 6 \frac{\text{joule}}{\text{coul}}$$

$$6 \text{ min} = 360 \text{ sec}$$

$$\left(5 \frac{\text{coul}}{\text{sec}}\right) \left(6 \frac{\text{joule}}{\text{coul}}\right) (360 \text{ sec}) = 11.8 \text{ kJ}$$

10.

$$\text{a) } I = \frac{\sum \mathcal{E}}{\sum R}$$

$$.001 = \frac{+3 - 2}{3 + 3 + R}$$

$$6 + R = 1000$$

$$R = 994 \Omega$$

$$\text{b) } P = i^2 R = (.001)^2 (994)$$

$$P = 9.9 \times 10^{-4} \text{ watts}$$

18.

First we need the currents.

$$\text{@ (d): } i_1 + i_3 - i_2 = 0$$

Left hand loop (LHL), cc (counter clockwise):

$$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$$

Right hand loop (RHL), cc:

$$-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$$

After some algebra:

$$i_1 = \frac{55}{200}, i_2 = \frac{5}{200}, i_3 = -\frac{50}{200}$$

$$V_d - V_c = ?$$

$$c \rightarrow d: V_d - V_c = i_2 R_2 = \left(\frac{5}{200}\right)(10) = .25 \text{ volts}$$

$$c \rightarrow b \rightarrow d: V_d - V_c = -\mathcal{E}_2 - i_3 R_3$$

$$V_d - V_c = -1 - \left(-\frac{50}{200}\right)(5) = .25 \text{ volts}$$

$$c \rightarrow b \rightarrow a \rightarrow d: V_d - V_c = -\mathcal{E}_2 + \mathcal{E}_1 - i_1 R_1$$

$$V_d - V_c = -1 + 4 - \left(\frac{55}{200}\right)(10) = .25 \text{ volts}$$

23.

At node N:

$$i_2 - i_3 - i_1 = 0$$

Top loop:

$$6V - 5V - 4V = 50i_2$$


$$i_2 = -\frac{3}{50} = -60 \text{ ma}$$

Bottom loop:

$$5V = 100i_1$$

$$i_1 = 50 \text{ ma}$$

$$V_{ab} = 5V + 4V = 9V$$

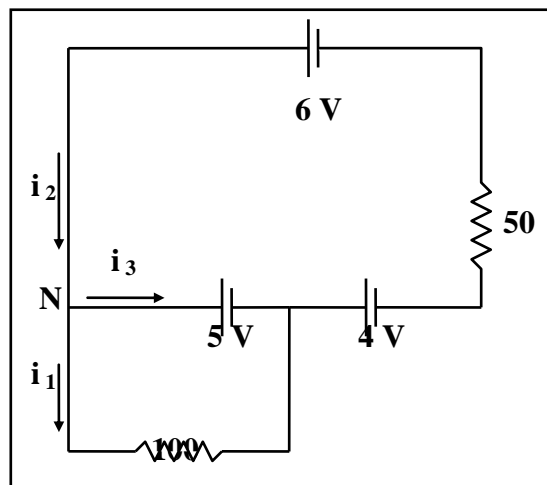

41.

At node N :

$$i_1 - i_2 + i_3 = 0$$

$$i_2 = i_1 + i_3 \quad (1)$$

LHL, cc :

$$3 - 4i_1 + 5i_3 = 0$$

$$4i_1 + 5i_3 = 3 \quad (2)$$

RHL, cc :

$$5i_3 - 2i_2 + 1 = 0$$

$$2i_2 + 5i_3 = 1 \quad (3)$$

$$2(i_1 + i_3) + 5i_3 = 1 \quad \text{sub(1)}$$

$$2i_1 + 7i_3 = 1$$

$$2(2i_1 + 7i_3 = 1)$$

$$+ (4i_1 + 5i_3 = 3) \quad (2)$$

$$19i_3 = 5$$

$$i_3 = .26 \text{amps}$$

$$i_2 = .16 \text{amps from (3)}$$

$$i_1 = .42 \text{amps from (2)}$$

$$c) P_1 = (i_1)^2 4 = .71$$

$$b) P_2 = (i_2)^2 2 = .051$$


$$a) P_3 = (i_3)^2 5 = .338$$

Power supplied by E_1 ?

$$d) P_1 = i_1 E_1 = (.42)(3) = 1.26$$

$$e) P_2 = i_2 E_2 = (.16)(1) = .16$$

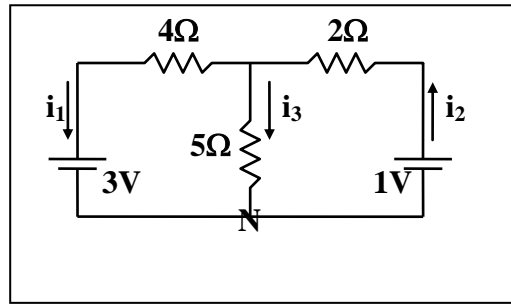The negative signs indicate the currents direction.



45.

At node N:

$$i_1 + i_2 + i_3 = 0$$

LHL, cw (clockwise):

$$+ 2 - 4 - 2i_1 + 2i_2 = 0$$

$$2 = -2i_1 + 2i_2$$

RHL, cc:

$$+ 4 - 4 - 2i_3 + 2i_2 = 0$$

$$\therefore i_3 = i_2$$

$$i_1 + i_2 + i_3 = i_1 + 2i_2 = 0$$

$$- 2i_1 + 2i_2 = 2$$

$$+ \quad - (i_1 + 2i_2) = 0$$

$$\hline - 3i_1 \quad = 2$$


$$i_1 = -\frac{2}{3} \text{ amps}$$

$$- 2i_1 + 2i_2 = 2 \Rightarrow i_2 = \frac{1}{3} \text{ amps}$$

$$i_3 = i_2 = \frac{1}{3} \text{ amps}$$

a) $V_a - 2(1/3) - 4 = V_b$

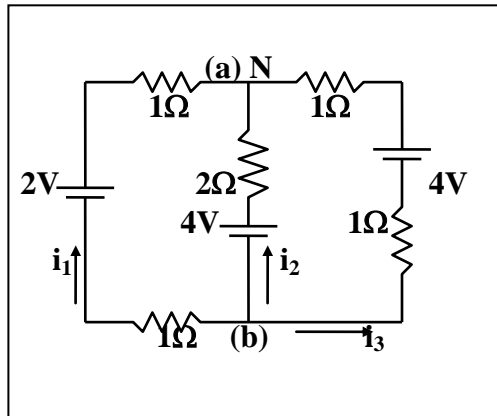b) $V_a - V_b = 4 - 2/3 = 3.3 \text{ volts}$



53.

Suppose $R_v = 0$.

$$i = \frac{\sum E}{\sum R} = \frac{3}{650} = .0046 \text{ amps}$$

Now put meter in parallel with R_1 .

$$\frac{1}{R_{eq}} = \frac{1}{250} + \frac{1}{5000}$$

$$R_{eq} = 238 \Omega$$

$$New\ i = \frac{\sum E}{\sum R} = \frac{3}{638} = .0047 \text{ amps}$$

With out volt meter :

$$V(R_1) = .0046(250) = 1.15 \text{ volts}$$

With volt meter :

$$V(R_1) = .0047(238) = 1.12 \text{ volts}$$

$$\frac{1.12 - 1.15}{1.15} = -2.6\%$$

58.

a) $t_c = \text{Time constant}$

$$t_c = RC = (1.4 \times 10^6 \Omega)(1.8 \times 10^{-6} \text{F})$$

$$t_c = 2.5 \text{ seconds}$$

b) As $t \rightarrow \infty$ $\exp\left[-\left(\frac{t}{RC}\right)\right] \rightarrow 0$

$$Q = C\mathcal{E} \left(1 - \exp\left[-\left(\frac{t}{RC}\right)\right]\right) \approx C\mathcal{E}$$

When t is large.

$$Q = C\mathcal{E} = (1.8 \mu\text{F})(12 \text{V}) = 21.6 \mu\text{C}$$

c) $Q = 16 \mu\text{C} = (21.6 \mu\text{C}) \left(1 - \exp\left[-\left(\frac{t}{RC}\right)\right]\right)$

$$.74 = 1 - \exp\left[-\left(\frac{t}{RC}\right)\right]$$

$$.26 = \exp\left[-\left(\frac{t}{RC}\right)\right]$$

$$\ln(.26) = -1.35 = -\frac{t}{RC}$$

$$\frac{t}{2.5} = 1.35$$

$$t = 3.36 \text{ seconds}$$

59.

Want $Q = (99\%)(Q_F)$.

$$Q = VC \left(1 - \exp \left[\left(-\frac{t}{RC} \right) \right] \right)$$

$$Q = Q_F \left(1 - \exp \left[\left(-\frac{t}{RC} \right) \right] \right)$$

$$.99Q_F = Q_F \left(1 - \exp \left[\left(-\frac{t}{RC} \right) \right] \right)$$

$$.99 = 1 - \exp \left[\left(-\frac{t}{RC} \right) \right]$$

$$.01 = \exp \left[\left(-\frac{t}{RC} \right) \right]$$

$$\ln(.01) = -4.6 = \left(-\frac{t}{RC} \right)$$

$$4.6 = \frac{t}{RC}$$

∴ It takes 4.6 time constants.

Units?

$$RC = \text{ohms} \cdot \text{farads} = \frac{\text{volts coulomb}}{\text{amps volts}}$$

$$RC = \frac{\text{coulomb}}{\text{amps}} = \left(\frac{\text{coulomb}}{\text{second}} \right) = \text{second}$$

78.

Suppose $R_A = 0$.

$$i = \frac{\sum \mathcal{E}}{\sum R} = \frac{5}{11} = .4545 \text{ amps}$$

With ammeter: $R_A = 0.10 \Omega$

$$i = \frac{\sum \mathcal{E}}{\sum R} = \frac{5}{11.1} = .4504 \text{ amps}$$

$$\frac{.4545 - .4504}{.4545} = .9\%$$

82.

$$V_{ac} = \mathcal{E}_2 - iR - ir_2$$

$$V_{ac} = 4.0 - .25(5) - .25(2)$$

$$V_{ac} = 2.25 \text{ volts}$$

90.

$$a) i = \frac{\mathcal{E}}{r + R}$$

Joule heating: $i^2 R$

$$P = i^2 R = \left(\frac{\mathcal{E}}{r + R} \right)^2 R = \frac{\mathcal{E}^2}{(r + R)^2} R$$

Maximize? $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = \frac{-2\mathcal{E}^2 R}{(r + R)^3} + \frac{\mathcal{E}^2}{(r + R)^2}$$

$$\frac{dP}{dR} = \frac{-2\mathcal{E}^2 R + \mathcal{E}^2(r + R)}{(r + R)^3} = \frac{\mathcal{E}^2(r - R)}{(r + R)^3}$$

$$\frac{dP}{dR} = 0 \Rightarrow r = R$$

$$b) P(R = r) = i^2 R = \frac{\mathcal{E}^2}{(r + R)^2} R = \frac{\mathcal{E}^2}{(r + r)^2} r$$

$$P = \frac{\mathcal{E}^2}{(2r)^2} r = \frac{\mathcal{E}^2}{4r}$$

Additional Problem

114. Power is a peak when $r = R$. See problem # 20

