

4.

$$U_E = \frac{1}{2} \frac{Q_m^2}{C}$$
$$1.40 \times 10^{-6} = \frac{1}{2} \frac{(1.6 \times 10^{-6})^2}{C}$$
$$C = \frac{(1.6 \times 10^{-6})^2}{2(1.40 \times 10^{-6})} = 9.14 \times 10^{-9}$$

5.

$$\frac{1}{2} \frac{Q_m^2}{C} = \frac{1}{2} L i_m^2$$
$$\frac{(3 \times 10^{-6})^2}{4 \times 10^{-6}} = (1.1 \times 10^{-3}) i_m^2$$
$$2.25 \times 10^{-6} = (1.1 \times 10^{-3}) i_m^2$$
$$i_m^2 = \frac{2.25 \times 10^{-6}}{(1.1 \times 10^{-3})} = 2.05 \times 10^{-3}$$
$$i_m = 45.2 \text{ mA}$$

11.

$$\text{a) } f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$
$$\frac{f_{\max}}{f_{\min}} = \frac{(LC_{\min})^{\frac{1}{2}}}{(LC_{\max})^{\frac{1}{2}}} = \sqrt{\frac{C_{\max}}{C_{\min}}}$$
$$\frac{f_{\max}}{f_{\min}} = \sqrt{\frac{365}{10}} = 6.04 \text{ or } 6 : 1$$
$$\text{b) } \frac{1.6}{.54} = \sqrt{\frac{365 + C}{10 + C}}$$
$$C = 35.63 \text{ pF}$$
$$v = \frac{\omega}{2\pi} = \frac{1}{2\pi} [L(C + 10)]^{\frac{1}{2}} = 1.6 \text{ MHz}$$
$$L = 2.2 \times 10^{-4} \text{ H}$$

13.

$$a) Q = Q_m \sin(\omega t)$$

$$I = \frac{dQ}{dt} = \omega Q_m \cos(\omega t)$$

$$I_m = \omega Q_m$$

$$Q_m = \frac{I_m}{\omega} = I_m \sqrt{LC}$$

$$Q_m = 2[(3 \times 10^{-3})(2.7 \times 10^{-6})]^{1/2}$$

$$Q_m = 1.8 \times 10^{-4} \text{ coulombs}$$

$$b) U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2C} Q_m^2 \sin^2(\omega t)$$

$$\frac{dU}{dt} = \frac{1}{2C} Q_m^2 [2 \sin(\omega t)(\omega \cos(\omega t))]$$

Use $2 \sin x \cos x = \sin 2x$

$$\frac{dU}{dt} = \frac{\omega Q_m^2}{2C} \sin(2\omega t)$$

Greatest rate occurs when $\sin(2\omega t) = 1$.

$$\text{So } \omega 2\omega t = \frac{\pi}{2} \text{ or } 2\left(\frac{2\pi}{T}\right)t = 2\pi$$

$$t = \frac{T}{8}$$

$$c) \text{ in eq. } \frac{dU}{dt} = \frac{\omega Q_m^2}{2C} \sin(2\omega t)$$

$$\omega = \frac{2\pi}{T} \text{ and } \sin(2\omega t) = 1$$

$$\left. \frac{dU}{dt} \right)_{\max} = \frac{\pi Q^2}{TC}$$

$$T = 2\pi\sqrt{LC} = 5.7 \times 10^{-4} \text{ sec}$$

$$\left. \frac{dU}{dt} \right)_{\max} = 66.7 \text{ watts}$$

29.

a) $V_L = V_{\max} \sin(\omega t)$

$$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{V_L}{L} = \frac{V_{\max} \sin(\omega t)}{L}$$

$$\int \frac{di}{dt} dt = \int \frac{V_{\max} \sin(\omega t)}{L} dt$$

$$i = -\frac{V_{\max}}{\omega L} \cos(\omega t) = -\frac{30}{(2\pi \times 10^3)(50 \times 10^{-3})} \cos(\omega t)$$

$i = .095$ amps

b) $i = -\frac{30}{(2\pi)(8 \times 10^3)(50 \times 10^{-3})} \cos(\omega t)$

$i = .0119$ amps

31.

a) $X_L = \omega L, X_C = \frac{1}{\omega C}$

$$\omega(6 \times 10^{-3}) = \frac{1}{\omega(10 \times 10^{-6})}$$

$$\omega^2 = \frac{1}{60 \times 10^{-9}}$$

$$\omega = 4.1 \times 10^3$$

$f = .65$ kHz

b) $X_L = \omega L = (4.1 \times 10^3)(6 \times 10^{-3})$

$X_L = 24.6 \Omega$

c) $f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{2\pi} \sqrt{\frac{1}{6 \times 10^{-8}}} = .65$ kHz

Same as part a).

32.

a) $X_L = \omega L = 377(12.7) = 4790 \Omega$

$$i_m = \frac{25}{4790} = .0052 \text{ amps}$$

b) Must be 90° out of phase or 0 volts.

c) $\mathcal{E} = -12.5$ @ $t = ?$

$$25 \sin(\omega t) = -12.5$$

$$\sin(\omega t) = \frac{1}{2} \Rightarrow \omega t = 30^\circ \text{ or } \frac{\pi}{6}$$

Since current must be out of phase with voltage.

$$I = I_m \cos\left(\frac{\pi}{6}\right) = .0052(.866) = 4.5 \text{ mA}$$

39. From sample problem 33-5

$$C = 15 \mu\text{F}$$

$$L = 230 \text{ H}$$

$$f = 60 \text{ Hz}$$

$$\mathcal{E}_m = 36 \text{ V}$$

$$R = 160 \Omega$$

remove inductor

$$Z = \sqrt{R^2 + (X_c)^2}$$

$$X_c = \frac{1}{\omega c} = \frac{1}{377(15 \times 10^{-6})} = 177 \Omega$$

$$Z = \sqrt{160^2 + 177^2} = 238.6 \Omega$$

$$I = \frac{\mathcal{E}}{Z} = \frac{36}{238.6} = .15 \text{ amps}$$

$$\tan \phi = \frac{-X_c}{R} = \frac{-177}{160} = -1.11$$

$$\phi = -47.9^\circ$$

47.

$$a) i_m = \frac{E_m}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

When is $\frac{di_m}{d\omega} = 0$?

$$\frac{di_m}{d\omega} = \frac{E_m}{2} \left[R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \right]^{-\frac{3}{2}} \left[2 \left(\omega L - \frac{1}{\omega C}\right) \left(L + \frac{1}{\omega^2 C}\right) \right]$$

$$\frac{di_m}{d\omega} = 0 \text{ when } \omega L - \frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{\sqrt{LC}} = \omega_0$$

$$\omega_0 = \left[1(20 \times 10^{-6}) \right]^{\frac{1}{2}} = 223.6 \frac{\text{rad}}{\text{sec}}$$

$$b) \text{max value } i = \frac{E_m}{R} = \frac{30}{5} = 6 \text{ amps}$$

$$c) \frac{1}{2} \frac{E_m}{R} = \frac{E_m}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$(2R)^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$3R^2 = \omega^2 L^2 - \frac{2L}{C} + \frac{1}{\omega^2 C^2}$$

Multiply thru by $\omega^2 C^2$ and collect like terms.

$$(L^2 C^2) \omega^4 - (3R^2 C^2 + 2LC) \omega^2 + 1 = 0$$

$$(4 \times 10^{-10}) \omega^4 - (3 \times 10^{-8} + 4 \times 10^{-5}) \omega^2 + 1 = 0$$

$$(4 \times 10^{-5}) \omega^4 - 4.003 \omega^2 + 10^5 = 0$$

Let $x = \omega^2$, then use the quadratic formula and positive ω 's.

$$x = 5.197 \times 10^4, 4.81 \times 10^4$$

$$\omega_1 = 227.98 \frac{\text{rad}}{\text{sec}}, \omega_2 = 219.32 \frac{\text{rad}}{\text{sec}}$$

$$d) \frac{\omega_1 - \omega_2}{\omega_0} = .0387$$

61.

$$\text{a) } i = i_m \sin(\omega t - \phi)$$

$$\cos \phi = \cos(-42^\circ) = .743$$

b) Since $\phi < 0$, i_m leads E .

$$\text{c) } \tan(-42^\circ) = -.9 = \frac{X_L - X_C}{R}$$

So $X_C > X_L$.

d) At resonance, $X_C = X_L \Rightarrow \tan \phi = 0$.

The circuit is not at resonance.

e) LR No

CR Possible

LCR Possible

$$\text{f) } P_{\text{AVE}} = \frac{1}{2} E_m i_m \cos \phi$$

$$P_{\text{AVE}} = (.5)(75)(1.2)(.743) = 33.4 \text{ watts}$$

g) The answers depend on the frequency used in the phase constant ϕ which is given.

66.

sample problem 7

$$r_t = \left(\frac{N_1}{N_2} \right)^2 R$$

power delivered to R

$$P_{\text{ave}} = i_2^2 R = \left(\frac{N_1}{N_2} i_1 \right)^2 R$$

using $i = \frac{\mathcal{E}}{R}$ and since total rest of amps is $r + r_t$

$$P_{\text{ave}} = \left(\frac{N_1}{N_2} \right)^2 \frac{\mathcal{E}_m^2 \sin^2 \omega t}{\left(r + \left(\frac{N_1}{N_2} \right)^2 R \right)^2} R$$

$$\text{let } x = \left(\frac{N_1}{N_2} \right)^2$$

$$P_{\text{ave}} = \frac{x}{(r + xR)^2} = x(r + xR)^{-2}$$

$$\frac{dP}{dx} = \frac{(r - xR)}{(r + xR)^3} = 0$$

$$\text{true if } x = \frac{r}{R} = \left(\frac{N_1}{N_2} \right)^2 = \frac{1000\Omega}{10\Omega}$$

$$\frac{N_1}{N_2} = 10$$

$$\frac{d}{dx} (x(r + xR)^{-2}) = (r + xR)^{-2} - 2x(r + xR)^{-3} R$$

$$= \frac{r + xR - 2xR}{(r + xR)^3} = \frac{r - xR}{(r + xR)^3}$$

Additional Problem

66.

$$P_{\text{AVE}} = (I_{\text{RMS}}^2)(R)$$

$$I_{\text{RMS}} = \left(\frac{C_{\text{RMS}}}{Z} \right)$$

$$P_{\text{AVE}} = \left(\frac{C_{\text{RMS}}}{Z} \right)^2 R$$

For a pure resistive circuit, $Z = R$.

$$P_{\text{AVE}} = \frac{C_{\text{RMS}}^2}{R}, \text{ O.K.}$$

Same for a RLC resonant circuit.

In a pure capacitive circuit, $R = 0$.

$$P_{\text{AVE}} = \left(\frac{C_{\text{RMS}}}{Z} \right)^2 R = 0$$

$\therefore P = 0$ O.K.